


ECE 1733: Switching Theory

Steve Brown

- Review of combinational circuits ✓
- " of sequential circuits
- Optimization of logic functions using algorithmic methods
 - Assign #1: implement a program that performs 2-level optimization
- Functional decomposition
- Binary Decision Diagrams (BDDs)
 - Assign #2: implement a "BDD Package".
- Boolean Satisfiability (SAT)
- Assign #3: paper summary presentation

Representation of Logic Functions

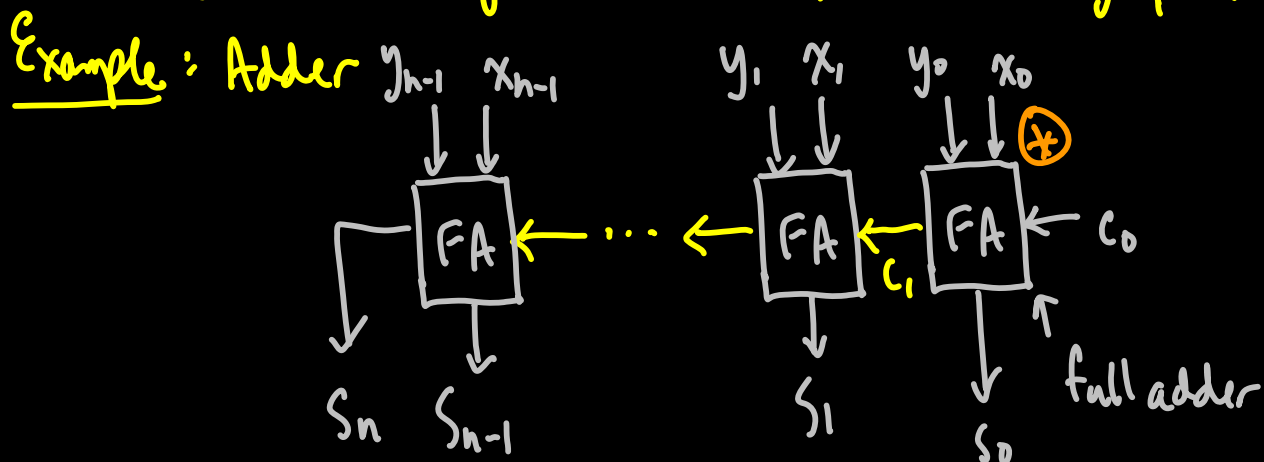Truth tables, sum-of-minterms (sum-of-products), Boolean expressions, Karnaugh maps, cubical notation, binary decision diagram (BDDs), and-inverter graph (AIG)



FA: Truth table (X)

C_0	y_0	x_0	C_1	S_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

minterms
 $m_0: \bar{C}_0 \bar{y}_0 \bar{x}_0$
 $m_1: \bar{C}_0 \bar{y}_0 x_0$

OR
 Sum-of-minterms

$$S_0 = \sum m(1, 2, 4, 7)$$

$$C_1 = \sum m(3, 5, 6, 7)$$

Boolean Expressions

Canonical S-o-f-l

$$S_0 = \bar{C}_0 \bar{y}_0 x_0 + \bar{C}_0 y_0 \bar{x}_0 + C_0 \bar{y}_0 \bar{x}_0 + C_0 y_0 x_0$$

$$C_1 = \bar{C}_0 y_0 x_0 + C_0 \bar{y}_0 x_0 + C_0 y_0 \bar{x}_0 + C_0 y_0 x_0$$

Karnaugh map

C_1

$C_0 y_0$	00	01	11	10
x_0				
0	0	0	1	0
1	0	1	0	1

$$C_1 = y_0 x_0 + C_0 x_0 + C_0 y_0 \quad (\text{majority function})$$

S_0

$C_0 y_0$	00	01	11	10
x_0				
0	0	1	0	1
1	1	0	1	0

$$S_0 = \bar{C}_0 \bar{y}_0 x_0 + \bar{C}_0 y_0 \bar{x}_0 + C_0 \bar{y}_0 \bar{x}_0 + C_0 y_0 x_0$$

$$S_0 = C_0 \oplus y_0 \oplus x_0 \quad (\text{odd function})$$

C_0	y_0	x_0	C_1	S_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$m_7: C_0 y_0 x_0$
 ↑
 AND

Boolean Algebra

Axioms: $0 \cdot 0 = 0$ (\cdot means AND)
 $1 + 1 = 1$ ($+$ means OR)
 \vdots

Rules: $x \cdot 0 = 0$
 $x + 1 = 1$
 \vdots
if $x = 0, \bar{x} = 1$ (" $-$ " means NOT, or
 $x = 1, \bar{x} = 0$ complement)

Identities:

$$\left. \begin{array}{l} x \cdot y = y \cdot x \\ x + y = y + x \end{array} \right\} \text{commutative}$$

$$\left. \begin{array}{l} x \cdot (y + z) = xy + xz \\ x + (y \cdot z) = (x + y) \cdot (x + z) \end{array} \right\} \text{distributive}$$

$$\left. \begin{array}{l} (x + y) + z = x + (y + z) \\ (x \cdot y) \cdot z = x \cdot (y \cdot z) \end{array} \right\} \text{associative}$$


$$\begin{array}{l} \rightarrow xy + x\bar{y} = x \\ \rightarrow (x + y) \cdot (x + \bar{y}) = x \end{array} \left. \vphantom{\begin{array}{l} \rightarrow xy + x\bar{y} = x \\ \rightarrow (x + y) \cdot (x + \bar{y}) = x \end{array}} \right\} \text{combining}$$

$$\hookrightarrow xx + xy + yx + y\bar{y} = x + xy = x$$

$$\left. \begin{array}{l} \overline{xy} = \bar{x} + \bar{y} \\ \overline{x + y} = \bar{x} \bar{y} \end{array} \right\} \text{De Morgan's theorem}$$

$$\begin{aligned} & \text{LTP } x \rightarrow y \Rightarrow \neg y \\ & \text{OR } x \rightarrow y \Rightarrow \neg y \end{aligned}$$

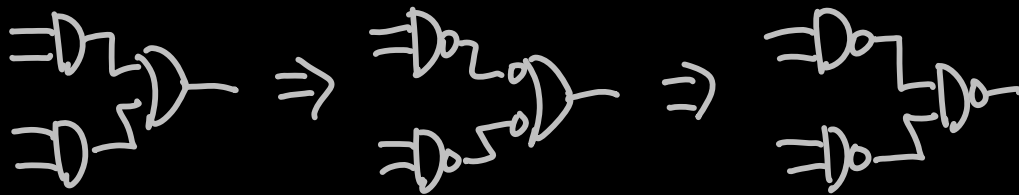- Using NAND Gates \Rightarrow 4 trans. \Rightarrow 6 trans.




Product-of-Sums (POS)

C_0	y_0	x_0	C_1	S_0	Maxterm
0	0	0	0	0	M_0 $C_0 + y_0 + x_0$
0	0	1	0	1	M_1 $C_0 + y_0 + \bar{x}_0$
0	1	0	0	1	\vdots
0	1	1	1	0	\vdots
1	0	0	0	1	\vdots
1	0	1	1	0	\vdots
1	1	0	1	0	\vdots
1	1	1	1	1	M_7 $\bar{C}_0 + \bar{y}_0 + \bar{x}_0$

$$\begin{aligned} \text{POS: } S_0 &= \prod M(0, 3, 5, 6) \\ C_1 &= \prod M(0, 1, 2, 4) \end{aligned}$$


C_1
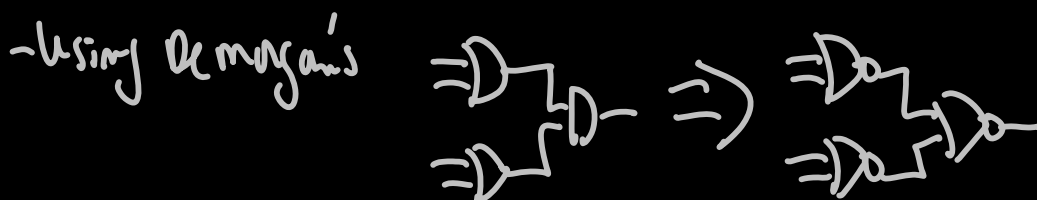
$$C_1 = (C_0 + x_0) \cdot (C_0 + y_0) \cdot (y_0 + x_0)$$



Using Boolean Algebra
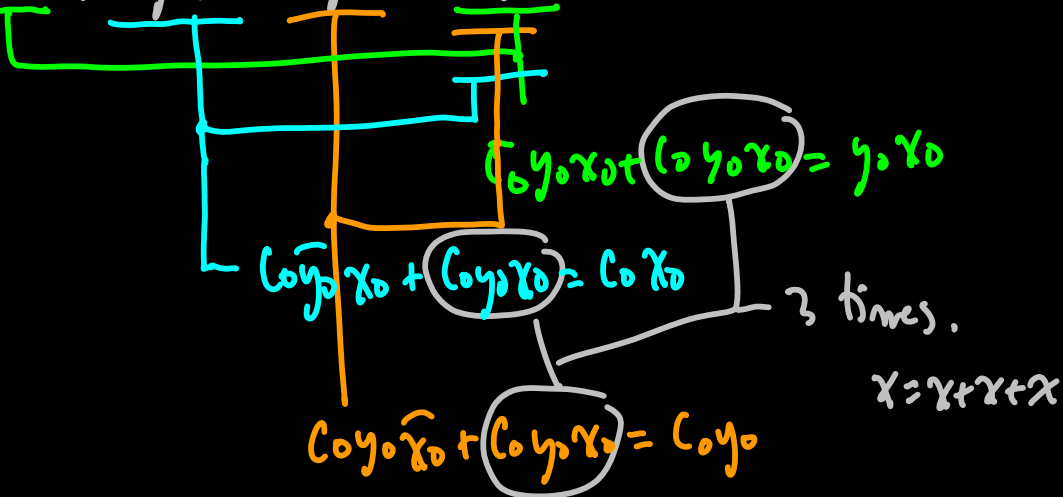
$$C_1 = \bar{C_0}y_0x_0 + C_0\bar{y}_0x_0 + C_0y_0\bar{x}_0 + C_0y_0x_0$$



Ex. $f = (\bar{x}_1\bar{x}_2) \cdot (x_3x_4) + (x_1+x_2) \cdot (x_3+x_4)$

- let $k = (x_1+x_2)$

$x = x + x\bar{y}$

then, $f = \bar{k} \cdot (x_3x_4) + k \cdot (x_3+x_4)$

$= \bar{k}x_3x_4 + kx_3 + kx_4$


$= \bar{k}x_3x_4 + kx_3x_4 + kx_3 + kx_4$

$= x_3x_4 + k(x_3+x_4)$

$= x_3x_4 + (x_1+x_2)(x_3+x_4)$

4-Variable k-map

$f(x_1, x_2, x_3, x_4)$

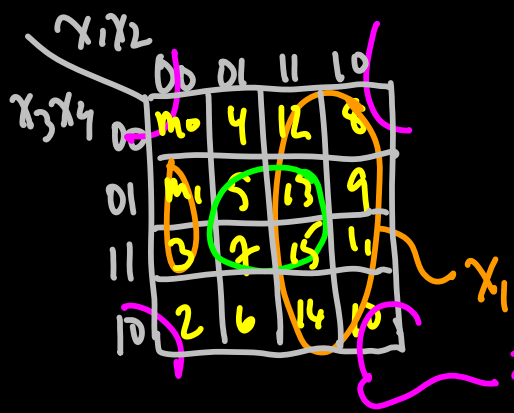


minterms

$x_1x_2x_3x_4$	
0000	m_0
0001	m_1
...	

$$m_1 + m_3 = \bar{x}_1 \bar{x}_2 \bar{x}_3 x_4 + \bar{x}_1 \bar{x}_2 x_3 x_4 = \bar{x}_1 \bar{x}_2 x_4$$

$$\begin{aligned} m_5 + m_7 + m_{13} + m_{15} &= \bar{x}_1 x_2 \bar{x}_3 x_4 + \bar{x}_1 x_2 x_3 x_4 + x_1 x_2 \bar{x}_3 x_4 + x_1 x_2 x_3 x_4 \\ &= x_2 x_4 (\bar{x}_1 \bar{x}_3 + \bar{x}_1 x_3 + x_1 \bar{x}_3 + x_1 x_3) \\ &= x_2 x_4 \end{aligned}$$

Example

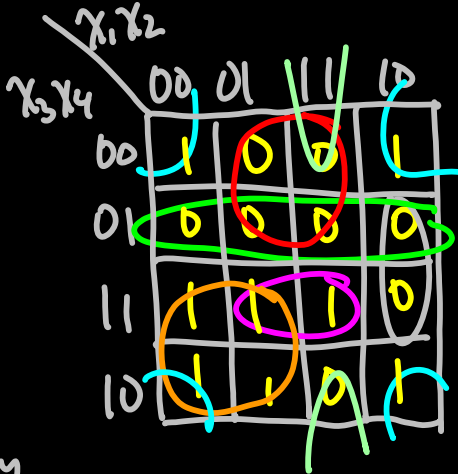

$$\text{SOP: } \bar{x}_1 x_3 + \bar{x}_2 \bar{x}_4 +$$

$$x_2 x_3 x_4$$

$$\begin{aligned} \text{POS: } & (x_3 + \bar{x}_4) \cdot (\bar{x}_2 + x_3) \cdot \\ & (\bar{x}_1 + x_2 + \bar{x}_4) \cdot \\ & (\bar{x}_1 + \bar{x}_2 + x_4) \end{aligned}$$

Terminology

Literal: a variable, or its complement

e.g. $x_1 \bar{x}_2$ has two literal

Implicant: for a given function, the implicants are the product terms that are covered by the function. e.g. minterms, groups of two 1's in k-map, groups of 4, ...

Prime Implicant: Informally: the biggest groups of 1's in a function's k-map.

Formally: any implicant for which it is not possible to remove any literal and still have a valid implicant


Essential PI : a PI that covers at least one minterm which is not covered by any other PI.

Cover : any sum of implicants that covers all of the minterms of a function.

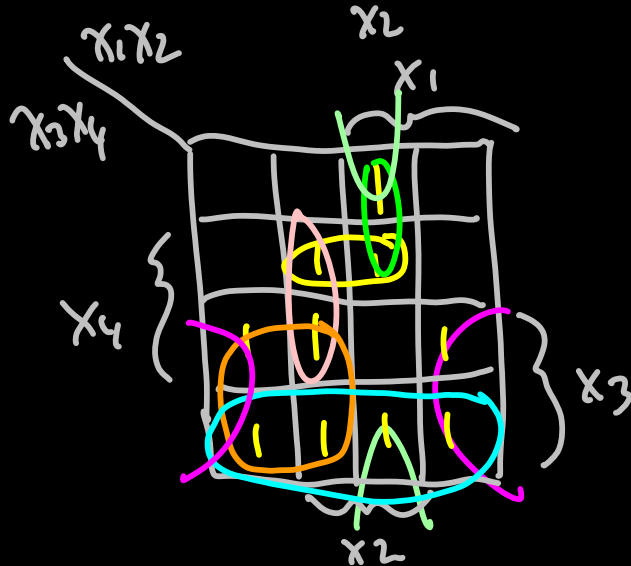Example



Implicants : $\{10 \text{ minterms}\}$,
groups of 2 1's $\{x_1 x_2 \bar{x}_3,$
 $x_2 \bar{x}_3 x_4, \bar{x}_1 x_2 x_4, \text{ plus}$
 $x_3 \text{ 11 others}\}, \bar{x}_1 x_3,$
 $x_3 \bar{x}_4, \bar{x}_2 x_3$



Prime Implicants : $\bar{x}_1 x_3, \bar{x}_2 x_3,$
 $x_3 \bar{x}_4, x_2 \bar{x}_3 x_4, x_1 x_2 \bar{x}_3,$
 $\bar{x}_1 x_2 x_4, x_1 x_2 \bar{x}_4$

Ess. PIs : $\bar{x}_2 x_3$


Cover : $\bar{x}_2 x_3, x_3 \bar{x}_4, x_1 x_2 \bar{x}_3, \bar{x}_1 x_2 x_4$

In general, we have to consider many (or even all) of PI choice-combinations to find the minimal cover(s).

Incompletely specified Logic Functions



Often, we know that some combinations of a function's inputs won't occur in practice, or if they do occur, we don't care about the function's output in that case. These cases are Don't Care inputs.

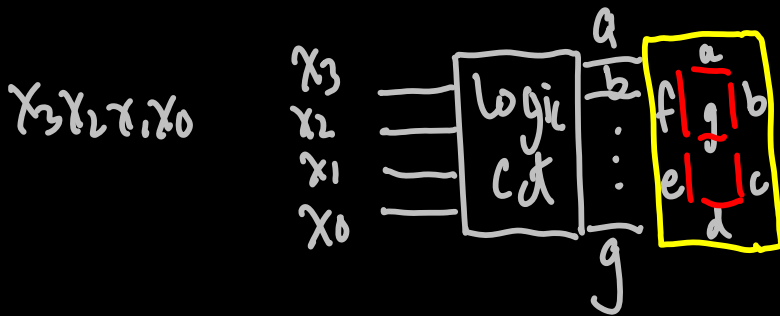Example: using binary-coded decimal (BCD)



$x_3 x_2 x_1 x_0$	a	...	e	f	g
0 0 0 0	1		0		
0 0 0 1	0		0		
0 0 1 0			0		
0 0 1 1	0		0		
0 1 0 0	0	...	0	...	
0 1 0 1	1		0		
0 1 1 0	1		0		
0 1 1 1	1		0		
1 0 0 0	1		0		
1 0 0 1	1		0		


k-map a

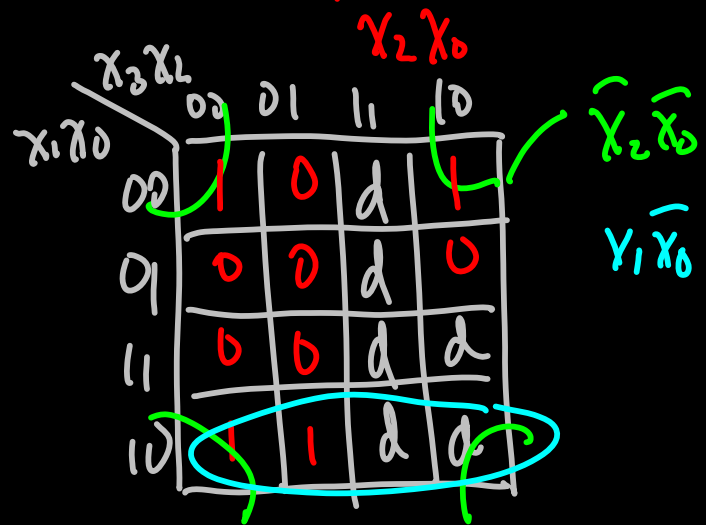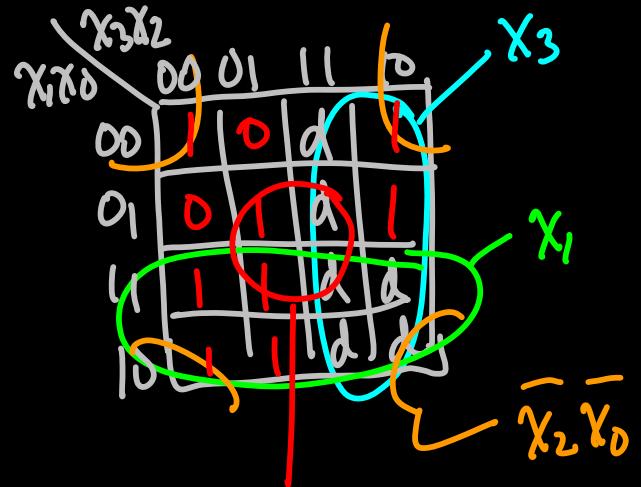

Sequential Circuits (review)

Def'n: a seq. ckt is one in which outputs depend on both the current and previous inputs. Hence, the ckt includes stored state information.

General model

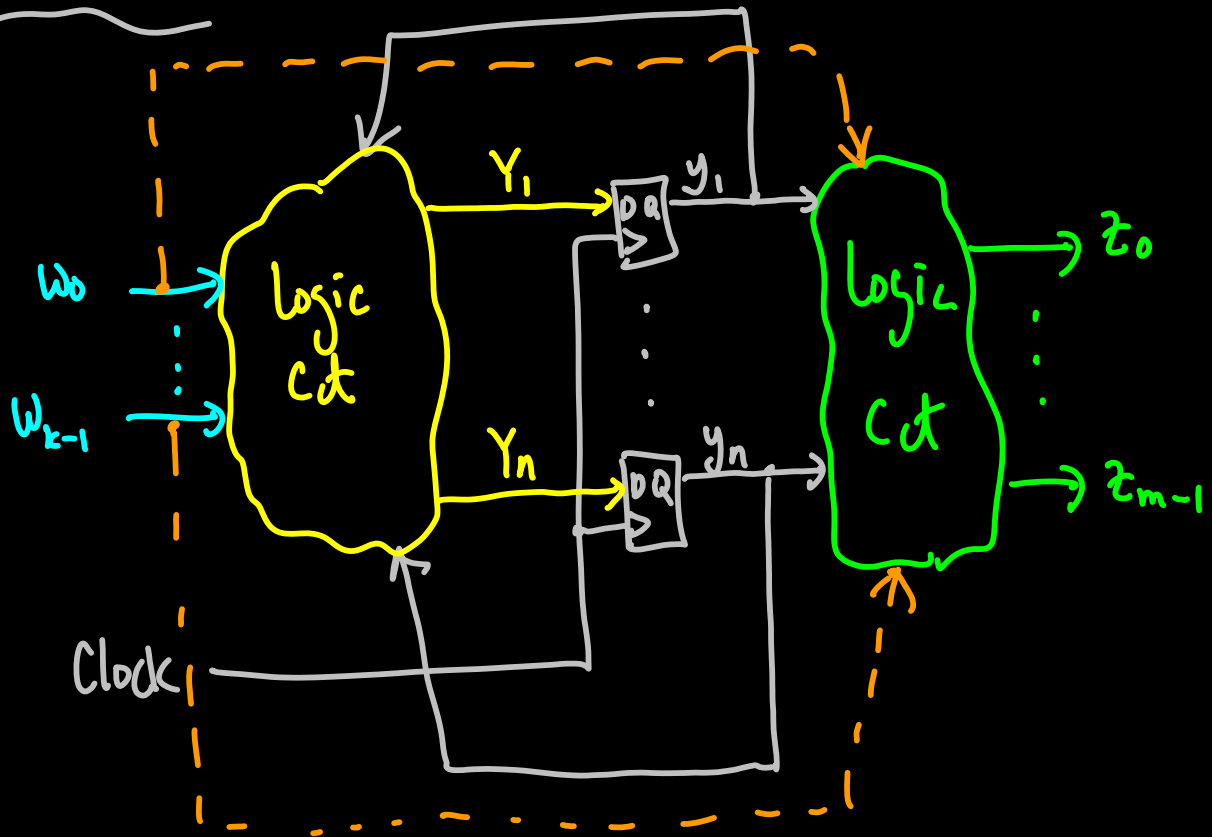

Seq. cts. are also called finite state machines (FSMs).


Moore-type FSM (w/o. --)

Mealy-type FSM (with --)


FSM Design Steps (review)

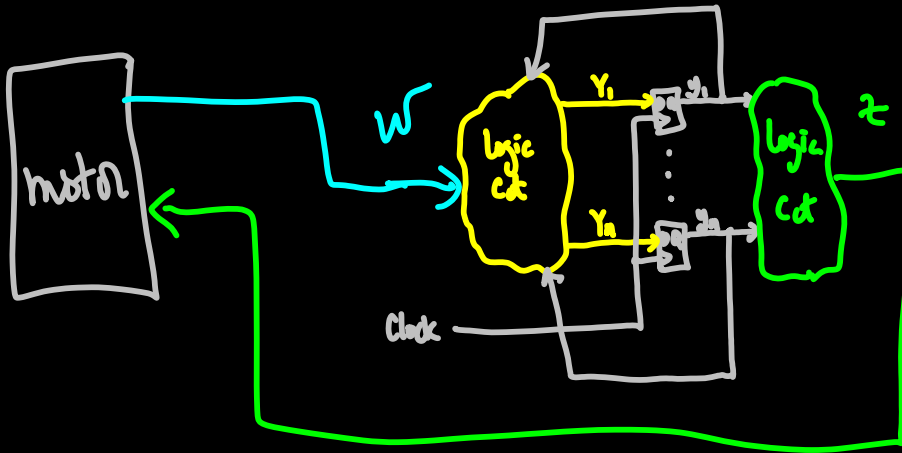Problem spec: design a ckt to control a motor. An input w is monitored by our FSM. If $w = 1, 0, 1$ over three clock cycles, then the motor has malfunctioned. Our FSM has to set an output $z = 1$ in the next clock cycle to reset the motor. Otherwise $z = 0$.

w 0 1 1 0 0 0 1 0 1 0 1 ...
 z 0 0 0 0 0 0 0 0 0 1 0 1 ...




1. State Diagram

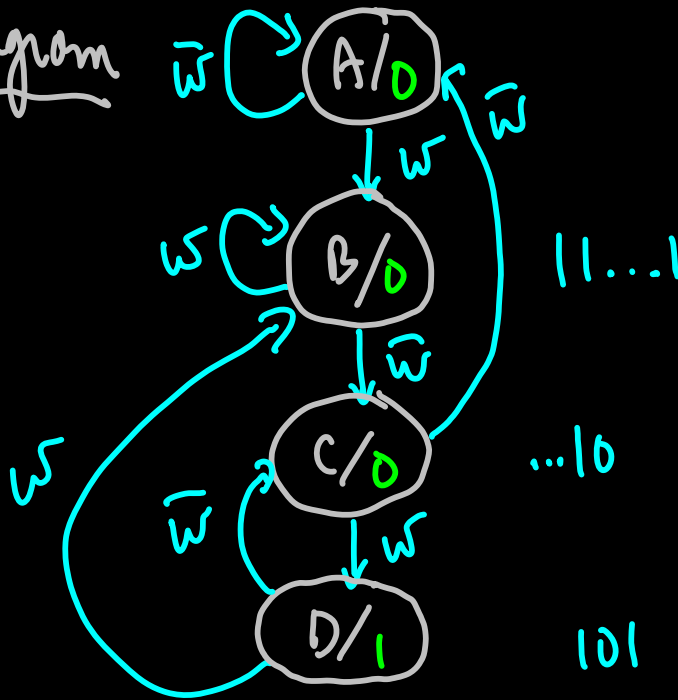

State Table

Present State	Next State		z
	$w=0$	$w=1$	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

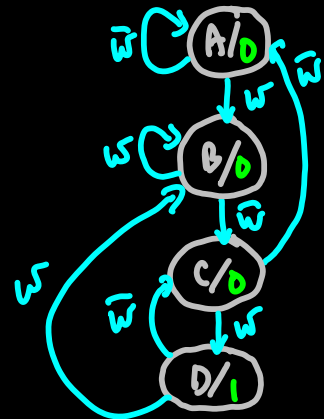

Choose the # of FFs.

Present state	Next state		z
	w=0	w=1	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

First choice: one FF for each state, with state codes

	y ₁	y ₂	y ₃	y ₄
A	1	0	0	0
B	0	1	0	0
C	0	0	1	0
D	0	0	0	1

one-hot encoding



$$Y_1 = \bar{w}y_1 + \bar{w}y_3 = \bar{w}(y_1 + y_3)$$

$$Y_2 = w(y_1 + y_2 + y_4)$$

$$Y_3 = \bar{w}(y_2 + y_4)$$

$$Y_4 = wy_3$$

$$z = y_4$$

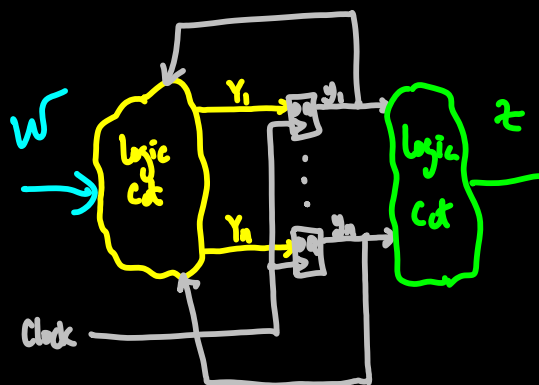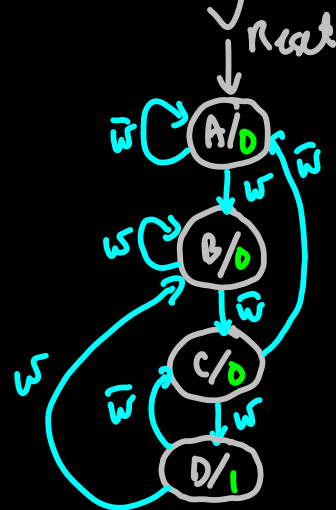


Second choice: minimum # of FF (2), with codes

	y ₁	y ₂
A	0	0
B	0	1
C	1	0
D	1	1

State-assigned Table

	PS $y_1 y_2$	NS		z
		$w=0$	$w=1$	
		$Y_1 Y_2$	$Y_1 Y_2$	
A	00	00	01	0
B	01	10	01	0
C	10	00	11	0
D	11	10	01	1

Present state	Next state		z
	$w=0$	$w=1$	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

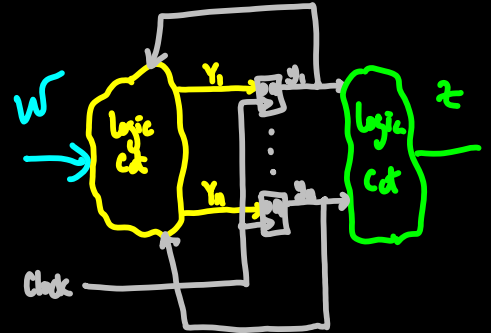


$Y_1:$

	w	0	1
$y_1 y_2$			
00		0	0
01		1	0
11		1	0
10		0	1


$\therefore Y_1 = \bar{w}y_2 + wy_1\bar{y}_2$
 $Y_2 = w$
 $z = y_1 y_2$

Third choice: use 3 FFs, with codes that correspond to the last three values of w .

Result (from intuition) will be:

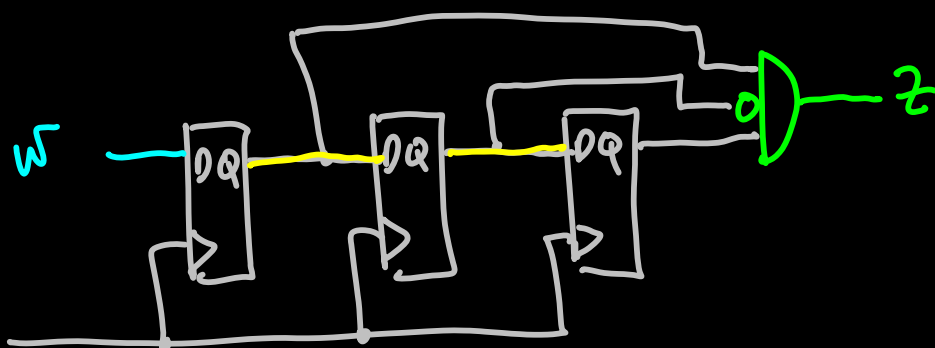

State Diagram

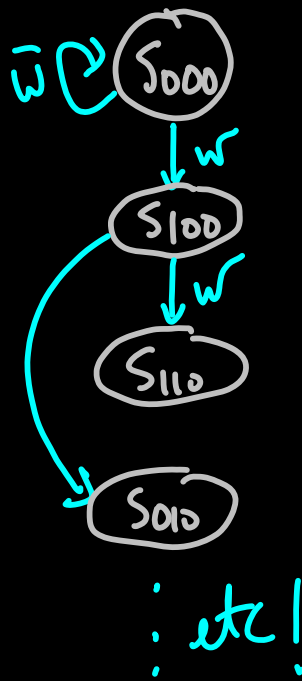

State Table

PS	NS		Z
	w=0	w=1	
S000	S000	S100	0
S001	S000	S100	0
S010	S001	S101	0
S011	S001	S101	0
S100	S010	S110	0
S101	S001	S110	1
S110	S011	S111	0
S111	S011	S111	0

- eventually we will get the shift register result.

State Minimization

- Given a set of states for an FSM, we can determine which states may be equivalent and are therefore not needed.

Def'n: for two states S_i, S_j , the states are equivalent if the FSM will produce an identical sequence of outputs independent of starting at S_i or S_j .

Example: Given the set of states $\{S_{000}, S_{001}, \dots, S_{111}\}$ from our previous example, find the minimum # of states


Step 1: partition states by output values

$$\{s_{000}, s_{001}, s_{010}, s_{011}, s_{100}, s_{110}, s_{111}\} \{s_{101}\}$$

Step 2: consider the 0-successors and 1-successors within each set.

s_{000}	s_{000}	s_{100}
s_{001}	s_{000}	s_{100}
s_{010}	s_{001}	s_{101}
s_{011}	s_{001}	s_{101}
s_{100}	s_{010}	s_{110}
s_{101}	s_{010}	s_{110}
s_{110}	s_{011}	s_{111}
s_{111}	s_{011}	s_{111}
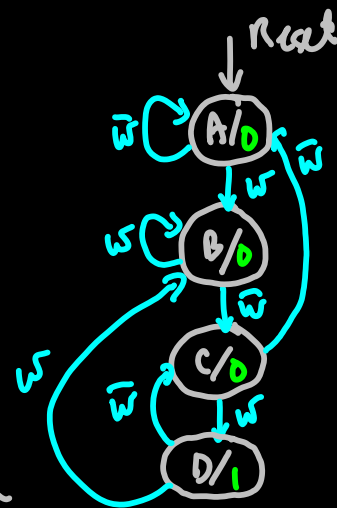
$$\begin{aligned} &\{s_{000}, s_{001}, s_{100}, s_{110}, s_{111}\} \{s_{101}\} \{s_{010}, s_{011}\} \\ &\{s_{000}, s_{001}\} \{s_{100}, s_{110}, s_{111}\} \{s_{101}\} \{s_{010}, s_{011}\} \\ &\quad A \quad B \quad C \quad D \end{aligned}$$



Algorithmic methods for Minimization

Definition:

Cube is an implicant (product term). A function can be represented as a set of cubes.

Example cubes: a cube is an n-tuple, where each digit can have three values: 0, 1, x. If a variable is uncomplemented in

the cube, then it is a 1; if complemented it is a 0; if that variable is not present, then it is x

<u>abcd</u>	<u>Cube</u>
$\bar{a}\bar{b}\bar{c}\bar{d}$	0000
$\bar{a}b\bar{c}\bar{d}$	1111
$a\bar{b}c$	101x
cd	xx11

$$f = bd + \bar{a}c\bar{d} + a\bar{b}c\bar{d} + \bar{a}d$$

$$= \{x1x1, 0x10, 1001, 0xx1\}$$

Quine-McCluskey

Step 1: arrange the minterms of the function by the cardinality of 1's

$$f = \sum m(1, 3, 5, 6, 7, 8, 14)$$

Def'n: Size of a cube is defined as the number of digits equal to x. 1010 (0-cube), x111 (1-cube), ...

	<u>a</u>	<u>b</u>	<u>c</u>	<u>d</u>						
1.	0	0	0	1	✓	(1,3)	00x1	✓	(1,3,5,7)	0xxx1
8.	1	0	0	0		(1,5)	0x01	✓	(1,5,3,7)	0xxx1
3.	0	0	1	1	✓	(3,7)	0x11	✓		
5.	0	1	0	1	✓	(5,7)	01x1	✓		
6.	0	1	1	0	✓	(6,7)	011x			
7.	0	1	1	1	✓	(6,14)	x110			
14	1	1	1	0	✓					

Step 2 : within each neighbouring group, try to combine all pairs of cubes (i.e., look for cubes that differ in one digit only)

- The result of this iterative procedure is the prime implicants of the function.

Step 3: draw a mintern cover table for selecting prime implicants. Identify the essential PIs

ρI	m_1	m_3	m_5	m_6	m_7	m_8	m_{14}
1000						✓	
011X				✓	✓		
X110				✓			✓
0XX1	✓	✓	✓		✓		

Here, the Ess. PTs are 1000, x110, 0xx1. These cover all minterms of f.

$$\therefore f = \{1000, x110, 0xx1\}$$

$$f = \sum m(0, 2, 3, 4, 6, 7, 9, 12, 13, 15, 16, 23, 24, 25, 29, 31)$$

00000 ✓	(0, 2)	000x0
00010 ✓	(0, 4)	00x00
00100 ✓	(0, 16)	x0000
10000 ✓	(2, 3)	0001x
00011 ✓	⋮	
00110		
01001		
01100		
11000		

⇒ Prime Implicants

00111
01101
11001
01111
10111
11101
11111

Step 2	0	2	3	4	6	7	9	12	13	15	16	23	24	25	29	31
00xx0	✓	✓		✓	✓						✓					
x0000	✓															
00x1x		✓	✓		✓	✓										
0x100				✓				✓								
1x000											✓		✓			
x1x01							✓	✓	✓					✓	✓	
0110x								✓	✓							
1100x													✓	✓		
xx111						✓				✓	✓	✓				✓
x11x1									✓	✓					✓	✓

Iteration: create a simplified table, removing the selected PIs and the covered minterms

	0	4	12	16	24
00xx0	✓	✓			
x0000	✓			✓	
0x100		✓	✓		
1x000				✓	✓
0110x			✓		
1100x					✓
x11x1					

Annotations: A cyan bracket on the right side of the first four rows is labeled "dominated". A magenta bracket on the right side of the last two rows is labeled "dominated". A cyan line under the last row is labeled "useless".

Row dominance: if one row dominates another, then delete the dominated row.

Redraw the simplified table:


	0	4	12	16	24
00xx0	✓	✓			
x0000	✓			✓	
0x100		✓	✓		
1x000				✓	✓

Annotations: The rows 0x100 and 1x000 are circled in green. The checkmarks in the 0x100 and 1x000 rows are also circled in green.

Now, we select "Essential PIs " 0x100, 1x000. Then, to cover m0 select 00xx0 (lower cost than x0000).

Note: for some cover tables, column dominance occurs:

	m_0	m_4	m_{12}	m_6	m_{24}
$00XX0$	✓	✓			
$X0000$	✓			✓	
$0X100$		✓	✓	✓	
$1X000$					✓

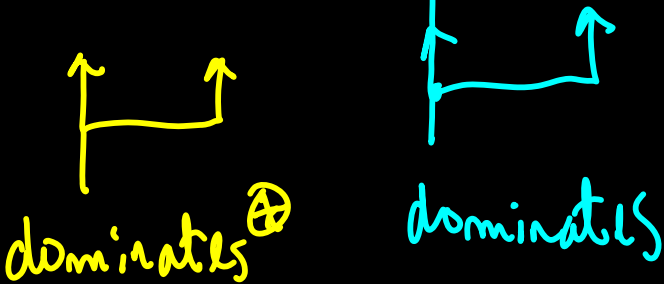

(*) the m_{12} column tells us that we need $0X100$.

Since this PI also covers m_4 , we don't need the m_4 column.

Summary

1. Generate all PIs from minterms through iterative combining
2. Create a cover table, and identify Ess. PIs.
3. if there are uncovered minterms, make a reduced cover table.
4. Use row/column dominance to reduce the cover table.

5. Identify new "Ess. PI s".

6. Iterate from step 3.

Note: It may be necessary to make "arbitrary" choices at the end. Example:

	m_i	m_j	m_k
PI_A	✓	✓	
PI_B		✓	✓
PI_C	✓		✓

- look at all combinations (branch & bound)

Using \times -operation and $\#$ -operation for minimization

\times -operation

- consider two 0-cubes (minterms) $A = 010, B = 110$

$A = 010 \quad A_1 \quad A_2 \quad A_3$

$B = 110 \quad B_1 \quad B_2 \quad B_3$

- two step \times -operation process:

(1) Use Table

$A_i \backslash B_i$	0	1	X
0	0	0	0
1	0	1	1
X	0	1	X

intuition: the \times -op table returns what A_i, B_i have "in common"

For our example $A_1 * B_1 = 0 * 1 = \emptyset$

$$A = 010$$

$$B = 110$$

$$A_2 * B_2 = 1 * 1 = 1$$

$$A_3 * B_3 = 0 * 0 = 0$$

Step 2: form the overall result $C = A * B$

Two cases: 1. $C = \emptyset$ if $A_i * B_i = \emptyset$ for more than one i .

2. Otherwise

$$C_i = A_i * B_i \text{ when } \neq \emptyset$$

$$C_i = x \text{ when } = \emptyset$$

Example:

$$A = 1x0, B = 1x1$$

$$A_1 * B_1 = 1$$

$$A_2 * B_2 = x$$

$$A_3 * B_3 = \emptyset$$

Case 2: $C = 1xx$

Algebraically: $A = x_1 \bar{x}_3$

$$B = x_1 x_3$$

$$A + B = x_1$$

Example:

$$A = 0x0$$

$$B = 1x1$$

$x_1 x_2$		x_3			
x_3		00	01	11	10
	0	1	1		
1				1	1

$$C = A * B = \emptyset$$

Example: $A = 0x0$
 $B = x11$ $\therefore C = A * B$
 $= 01\bar{x}$

$$A_1 * B_1 = 0$$

$$A_2 * B_2 = 1$$

$$A_3 * B_3 = \phi$$

$x_1 x_2$		00	01	11	10
x_3	0	1	1		
	1		1	1	

- The $*$ -operation can be used to generate all implicants, and therefore all prime implicants.