


# ECE 1733: Switching Theory

Steve Brown

- Review of combinational circuits ✓
- " of sequential circuits
- Optimization of logic functions using algorithmic methods
  - Assign #1: implement a program that performs 2-level optimization
- Functional decomposition
- Binary Decision Diagrams (BDDs)
  - Assign #2: implement a "BDD Package".
- Boolean Satisfiability (SAT)
- Assign #3: paper summary presentation
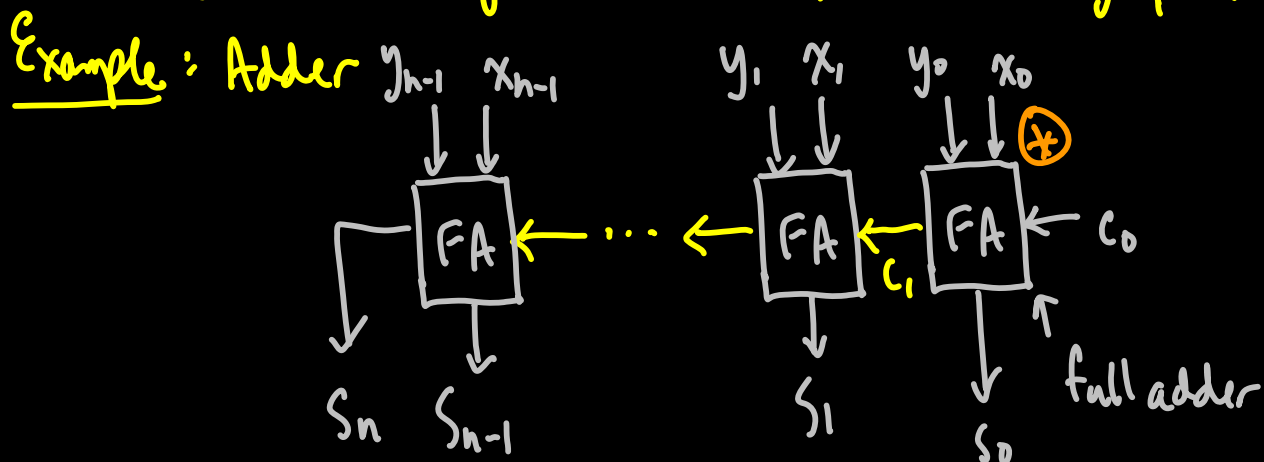
## Representation of Logic Functions

Truth tables, sum-of-minterms (sum-of-products), Boolean expressions, Karnaugh maps, cubical notation, binary decision diagram (BDDs), and-inverter graph (AIG)



FA: Truth table (X)

$C_0$	$y_0$	$x_0$	$C_1$	$S_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

minterms  
 $m_0: \bar{C}_0 \bar{y}_0 \bar{x}_0$   
 $m_1: \bar{C}_0 \bar{y}_0 x_0$

OR  
 Sum-of-minterms

$$S_0 = \sum m(1, 2, 4, 7)$$

$$C_1 = \sum m(3, 5, 6, 7)$$

Boolean Expressions

Canonical S-o-f-l

$$S_0 = \bar{C}_0 \bar{y}_0 x_0 + \bar{C}_0 y_0 \bar{x}_0 + C_0 \bar{y}_0 \bar{x}_0 + C_0 y_0 x_0$$

$$C_1 = \bar{C}_0 y_0 x_0 + C_0 \bar{y}_0 x_0 + C_0 y_0 \bar{x}_0 + C_0 y_0 x_0$$

Karnaugh map

$C_1$

$C_0 y_0$	00	01	11	10
$x_0$				
0	0	0	1	0
1	0	1	0	1

$$C_1 = y_0 x_0 + C_0 x_0 + C_0 y_0 \quad (\text{majority function})$$

$S_0$

$C_0 y_0$	00	01	11	10
$x_0$				
0	0	1	0	1
1	1	0	1	0

$$S_0 = \bar{C}_0 \bar{y}_0 x_0 + \bar{C}_0 y_0 \bar{x}_0 + C_0 \bar{y}_0 \bar{x}_0 + C_0 y_0 x_0$$

$$S_0 = C_0 \oplus y_0 \oplus x_0 \quad (\text{odd function})$$

$C_0$	$y_0$	$x_0$	$C_1$	$S_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$m_7: C_0 y_0 x_0$   
 ↑  
 AND

# Boolean Algebra

Axioms:  $0 \cdot 0 = 0$  ( $\cdot$  means AND)  
 $1 + 1 = 1$  ( $+$  means OR)  
 $\vdots$

Rules:  $x \cdot 0 = 0$   
 $x + 1 = 1$   
 $\vdots$   
if  $x = 0, \bar{x} = 1$  (" $-$ " means NOT, or  
 $x = 1, \bar{x} = 0$  complement)

## Identities:

$$\left. \begin{array}{l} x \cdot y = y \cdot x \\ x + y = y + x \end{array} \right\} \text{commutative}$$

$$\left. \begin{array}{l} x \cdot (y + z) = xy + xz \\ x + (y \cdot z) = (x + y) \cdot (x + z) \end{array} \right\} \text{distributive}$$

$$\left. \begin{array}{l} (x + y) + z = x + (y + z) \\ (x \cdot y) \cdot z = x \cdot (y \cdot z) \end{array} \right\} \text{associative}$$


$$\begin{array}{l} \rightarrow xy + x\bar{y} = x \\ \rightarrow (x + y) \cdot (x + \bar{y}) = x \end{array} \left. \vphantom{\begin{array}{l} \rightarrow xy + x\bar{y} = x \\ \rightarrow (x + y) \cdot (x + \bar{y}) = x \end{array}} \right\} \text{combining}$$

$$\hookrightarrow x\bar{x} + x\bar{y} + y\bar{x} + y\bar{y} = x + x\bar{y} = x$$

$$\left. \begin{array}{l} \overline{xy} = \bar{x} + \bar{y} \\ \overline{x + y} = \bar{x} \bar{y} \end{array} \right\} \text{De Morgan's theorem}$$

$$\begin{aligned} & \text{LTP } x \rightarrow y \Rightarrow \neg y \\ & \text{LTP } y \rightarrow x \Rightarrow \neg x \end{aligned}$$

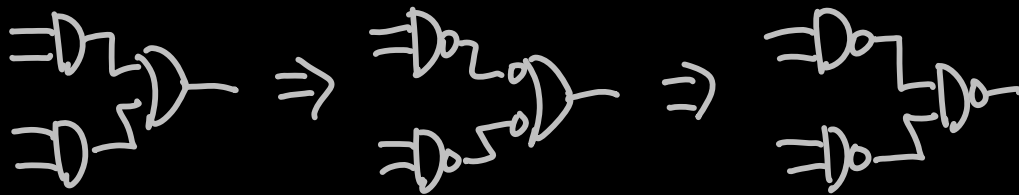- Using NAND Gates  $\Rightarrow$  4 trans.  $\Rightarrow$  6 trans.




## Product-of-Sums (POS)

$C_0$	$y_0$	$x_0$	$C_1$	$S_0$	Maxterm
0	0	0	0	0	$M_0$ $C_0 + y_0 + x_0$
0	0	1	0	1	$M_1$ $C_0 + y_0 + \bar{x}_0$
0	1	0	0	1	$\vdots$
0	1	1	1	0	$\vdots$
1	0	0	0	1	$\vdots$
1	0	1	1	0	$\vdots$
1	1	0	1	0	$\vdots$
1	1	1	1	1	$M_7$ $\bar{C}_0 + \bar{y}_0 + \bar{x}_0$

$$\begin{aligned} \text{POS: } S_0 &= \prod M(0, 3, 5, 6) \\ C_1 &= \prod M(0, 1, 2, 4) \end{aligned}$$


$C_1$
 
$$C_1 = (C_0 + x_0) \cdot (C_0 + y_0) \cdot (y_0 + x_0)$$


 
# Using Boolean Algebra

$$C_1 = \bar{C_0}y_0x_0 + C_0\bar{y}_0x_0 + C_0y_0\bar{x}_0 + C_0y_0x_0$$



Ex.  $f = (\bar{x}_1\bar{x}_2) \cdot (x_3x_4) + (x_1+x_2) \cdot (x_3+x_4)$

- let  $k = (x_1+x_2)$

$x = x + x\bar{y}$

then,  $f = \bar{k} \cdot (x_3x_4) + k \cdot (x_3+x_4)$

$= \bar{k}x_3x_4 + kx_3 + kx_4$


$= \bar{k}x_3x_4 + kx_3x_4 + kx_3 + kx_4$

$= x_3x_4 + k(x_3+x_4)$

$= x_3x_4 + (x_1+x_2)(x_3+x_4)$

## 4-Variable k-map

$f(x_1, x_2, x_3, x_4)$

 

## minterms


$x_1x_2x_3x_4$

0	0	0	0	$m_0$
0	0	0	1	$m_1$
				$\vdots$

$$m_1 + m_3 = \bar{x}_1 \bar{x}_2 \bar{x}_3 x_4 + \bar{x}_1 \bar{x}_2 x_3 x_4 = \bar{x}_1 \bar{x}_2 x_4$$

$$\begin{aligned} m_5 + m_7 + m_{13} + m_{15} &= \bar{x}_1 x_2 \bar{x}_3 x_4 + \bar{x}_1 x_2 x_3 x_4 + x_1 x_2 \bar{x}_3 x_4 + x_1 x_2 x_3 x_4 \\ &= x_2 x_4 (\bar{x}_1 \bar{x}_3 + \bar{x}_1 x_3 + x_1 \bar{x}_3 + x_1 x_3) \\ &= x_2 x_4 \end{aligned}$$

Example

 

$$\text{SOP: } \bar{x}_1 x_3 + \bar{x}_2 \bar{x}_4 +$$

$$x_2 x_3 x_4$$

$$\begin{aligned} \text{POS: } & (x_3 + \bar{x}_4) \cdot (\bar{x}_2 + x_3) \cdot \\ & (\bar{x}_1 + x_2 + \bar{x}_4) \cdot \\ & (\bar{x}_1 + \bar{x}_2 + x_4) \end{aligned}$$

Terminology

Literal: a variable, or its complement

e.g.  $x_1 \bar{x}_2$  has two literal

Implicant: for a given function, the implicants are the product terms that are covered by the function. e.g. minterms, groups of two 1's in k-map, groups of 4, ...


Prime Implicant: Informally: the biggest groups of 1's in a function's k-map.

Formally: any implicant for which it is not possible to remove any literal and still have a valid implicant


Essential PI : a PI that covers at least one minterm which is not covered by any other PI.

Cover : any sum of implicants that covers all of the minterms of a function.

Example

 

 Implicants :  $\{10 \text{ minterms}\}$ ,  
groups of 2 1's  $\{x_1x_2\bar{x}_3,$   
 $x_2\bar{x}_3x_4, \bar{x}_1x_2x_4, \text{ plus}$   
 $x_3 \text{ 11 others}\}, \bar{x}_1x_3,$   
 $x_3\bar{x}_4, \bar{x}_2x_3$



Prime Implicants :  $\bar{x}_1x_3, \bar{x}_2x_3,$   
 $x_3\bar{x}_4, x_2\bar{x}_3x_4, x_1x_2\bar{x}_3,$   
 $\bar{x}_1x_2x_4, x_1x_2\bar{x}_4$

Ess. PIs :  $\bar{x}_2x_3$


Cover :  $\bar{x}_2x_3, x_3\bar{x}_4, x_1x_2\bar{x}_3, \bar{x}_1x_2x_4$

In general, we have to consider many (or even all) of PI choice-combinations to find the minimal cover(s).

# Incompletely specified Logic Functions



Often, we know that some combinations of a function's inputs won't occur in practice, or if they do occur, we don't care about the function's output in that case. These cases are Don't Care inputs.

 Example: using binary-coded decimal (BCD)



$x_3 x_2 x_1 x_0$	a	...	e	f	g
0 0 0 0	1		0		
0 0 0 1	0		0		
0 0 1 0			0		
0 0 1 1	0		0		
0 1 0 0	0	...	0	...	
0 1 0 1	1		0		
0 1 1 0	1		0		
0 1 1 1	1		0		
1 0 0 0	1		0		
1 0 0 1	1		0		

k-map a

  


## Sequential Circuits (review)

Def'n: a seq. ckt is one in which outputs depend on both the current and previous inputs. Hence, the ckt includes stored state information.



## General model

 

Seq. cts. are also called finite state machines (FSMs).


Moore-type FSM (w/o --)

Mealy-type FSM (with --)

## FSM Design Steps (review)

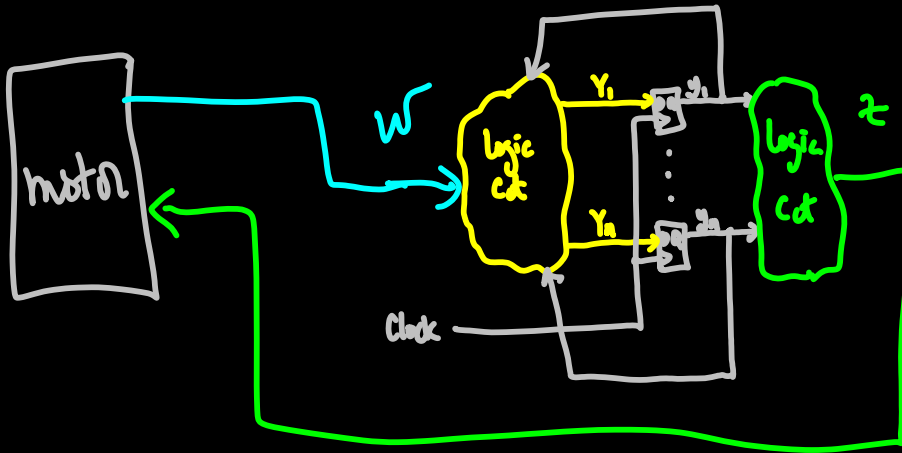
Problem spec: design a ckt to control a motor. An input  $w$  is monitored by our FSM. If  $w = 1, 0, 1$  over three clock cycles, then the motor has malfunctioned. Our FSM has to set an output  $\tau = 1$  in the next clock cycle to reset the motor. Otherwise  $\tau = 0$ .

$w$  0 1 1 0 0 0 1 0 1 0 1 ...  
 $z$  0 0 0 0 0 0 0 0 0 1 0 1 ...




101

# 1. State Diagram

 

## State Table

Present State	Next State		z
	w=0	w=1	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

 


Choose the # of FFs.

Present state	Next state		z
	w=0	w=1	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

First choice: one FF for each state, with state codes

	y <sub>1</sub>	y <sub>2</sub>	y <sub>3</sub>	y <sub>4</sub>
A	1	0	0	0
B	0	1	0	0
C	0	0	1	0
D	0	0	0	1

one-hot encoding

 


$$Y_1 = \bar{w}y_1 + \bar{w}y_3 = \bar{w}(y_1 + y_3)$$

$$Y_2 = w(y_1 + y_2 + y_4)$$

$$Y_3 = \bar{w}(y_2 + y_4)$$

$$Y_4 = wy_3$$

$$z = y_4$$

 


Second choice: minimum # of FF (2), with codes

	$y_1$	$y_2$
A	0	0
B	0	1
C	1	0
D	1	1

# State-assigned Table

	PS $y_1 y_2$	NS		$z$
		$w=0$	$w=1$	
		$Y_1 Y_2$	$Y_1 Y_2$	
A	00	00	01	0
B	01	10	01	0
C	10	00	11	0
D	11	10	01	1

Present state	Next state		$z$
	$w=0$	$w=1$	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

 

$Y_1:$ 


	$w$	0	1
$y_1 y_2$			
00		0	0
01		1	0
11		1	0
10		0	1

 $\therefore Y_1 = \bar{w}y_2 + wy_1\bar{y}_2$


$\bar{w}y_2$  (points to the 01 and 11 rows in the table)  
 $wy_1\bar{y}_2$  (points to the 10 row in the table)  
 $Y_2 = w$   
 $z = y_1 y_2$

Third choice: use 3 FFs, with codes that correspond to the last three values of  $w$ .

Result (from intuition) will be:

 

## State Diagram

 

## State Table

$P_S$	$NS$		$z$
	$w=0$	$w=1$	
$S_{000}$	$S_{000}$	$S_{100}$	0
$S_{001}$	$S_{000}$	$S_{100}$	0
$S_{010}$	$S_{001}$	$S_{101}$	0
$S_{011}$	$S_{001}$	$S_{101}$	0
$S_{100}$	$S_{010}$	$S_{110}$	0
$S_{101}$	$S_{001}$	$S_{110}$	1
$S_{110}$	$S_{011}$	$S_{111}$	0
$S_{111}$	$S_{011}$	$S_{111}$	0

- eventually we will get the shift register result.

## State Minimization

- Given a set of states for an FSM, we can determine which states may be equivalent and are therefore not needed.

Def'n: for two states  $S_i, S_j$ , the states are equivalent if the FSM will produce an identical sequence of outputs independent of starting at  $S_i$  or  $S_j$ .

Example: Given the set of states  $\{S_{000}, S_{001}, \dots, S_{111}\}$  from our previous example, find the minimum # of states

Step 1: partition states by output values

$$\{s_{000}, s_{001}, s_{010}, s_{011}, s_{100}, s_{110}, s_{111}\} \{s_{101}\}$$


Step 2: consider the 0-successors and 1-successors within each set.

$s_{000}$	$s_{000}$	$s_{100}$
$s_{001}$	$s_{000}$	$s_{100}$
$s_{010}$	$s_{001}$	$s_{101}$
$s_{011}$	$s_{001}$	$s_{101}$
$s_{100}$	$s_{010}$	$s_{110}$
$s_{101}$	$s_{010}$	$s_{110}$
$s_{110}$	$s_{011}$	$s_{111}$
$s_{111}$	$s_{011}$	$s_{111}$

$$\{s_{000}, s_{001}, s_{100}, s_{110}, s_{111}\} \{s_{101}\} \{s_{010}, s_{011}\}$$

$$\{s_{000}, s_{001}\} \{s_{100}, s_{110}, s_{111}\} \{s_{101}\} \{s_{010}, s_{011}\}$$

 A                      B                      C                      D



## Algorithmic methods for Minimization

Definition:

Cube is an implicant (product term). A function can be represented as a set of cubes

Example cubes: a cube is an n-tuple, where each digit can have three values: 0, 1, x  
If a variable is uncomplemented in

the cube, then it is a 1; if complemented it is a 0; if that variable is not present, then it is x

<u>abcd</u>	<u>Cube</u>
$\bar{a}\bar{b}\bar{c}\bar{d}$	0000
$\bar{a}b\bar{c}\bar{d}$	1111
$a\bar{b}c$	101x
$cd$	xx11

$$f = bd + \bar{a}c\bar{d} + a\bar{b}c\bar{d} + \bar{a}d$$

$$= \{x1x1, 0x10, 1001, 0xx1\}$$

### Quine-McCluskey

Step 1: arrange the minterms of the function by the cardinality of 1's

$$f = \sum m(1, 3, 5, 6, 7, 8, 14)$$

Def'n: Size of a cube is defined as the number of digits equal to x. 1010 (0-cube), x111 (1-cube), ...

	<u>a</u>	<u>b</u>	<u>c</u>	<u>d</u>				
1.	0	0	0	1	✓	(1,3)	00x1	✓
8.	1	0	0	0		(1,5)	0x01	✓
3.	0	0	1	1	✓	(3,7)	0x11	✓
5.	0	1	0	1	✓	(5,7)	01x1	✓
6.	0	1	1	0	✓	(6,7)	011x	
7.	0	1	1	1	✓	(6,14)	x110	
14	1	1	1	0	✓			

Step 2 : within each neighbouring group, try to combine all pairs of cubes (i.e., look for cubes that differ in one digit only)

- The result of this iterative procedure is the prime implicants of the function.

Step 3: draw a mintern cover table for selecting prime implicants. Identify the essential PIs

$\rho_I$	$m_1$	$m_3$	$m_5$	$m_6$	$m_7$	$m_8$	$m_{14}$
1000						✓	
011X				✓	✓		
X110				✓			✓
0XX1	✓	✓	✓		✓		



Here, the Ess. PTs are 1000, x110, 0xx1. These cover all minterms of f.

$$\therefore f = \{1000, x110, 0xx1\}$$

$$f = \sum m(0, 2, 3, 4, 6, 7, 9, 12, 13, 15, 16, 23, 24, 25, 29, 31)$$

00000 ✓  
 00010 ✓  
 00100 ✓  
 10000 ✓  
 00011 ✓  
 00110  
 01001  
 01100  
 11000  
 00111  
 01101  
 11001  
 01111  
 10111  
 11101  
 11111

(0, 2) 000x0  
 (0, 4) 00x00  
 (0, 16) x0000  
 (2, 3) 0001x  
 ⋮

⇒ Prime Implicants

Step 2	0	2	3	4	6	7	9	12	13	15	16	23	24	25	29	31
00xx0	✓	✓		✓	✓											
x0000	✓										✓					
00x1x		✓	✓		✓	✓										
0x100				✓				✓								
1x000											✓		✓			
x1x01							✓	✓						✓	✓	
0110x								✓	✓							
1100x													✓	✓		
xx111						✓				✓	✓	✓				✓
x11x1								✓	✓						✓	✓

Iteration: create a simplified table, removing the selected  $PIs$  and the covered minterms

	0	4	12	16	24
00xx0	✓	✓			
x0000	✓			✓	
0x100		✓	✓		
1x000				✓	✓
<del>0110x</del>			✓		
<del>1100x</del>					✓
<del>x11x1</del>					

Annotations: A cyan bracket on the right side of the first four rows is labeled "dominated". A magenta bracket on the right side of the last two rows is labeled "dominated". A cyan line under the last row is labeled "useless".

Row dominance: if one row dominates another, then delete the dominated row.

Redraw the simplified table:


	0	4	12	16	24
00xx0	✓	✓			
x0000	✓			✓	
0x100		✓	✓		
1x000				✓	✓

Annotations: The rows 0x100 and 1x000 are circled in green. The checkmarks in the 0x100 and 1x000 rows for columns 4, 12, 16, and 24 are also circled in green.

Now, we select "Essential  $PIs$ " 0x100, 1x000. Then, to cover  $m_0$  select 00xx0 (lower cost than x0000).

Note: for some cover tables, column dominance occurs:

	$m_0$	$m_4$	$m_{12}$	$m_6$	$m_{24}$
$00XX0$	✓	✓			
$X0000$	✓			✓	
$0X100$		✓	✓	✓	
$1X000$					✓

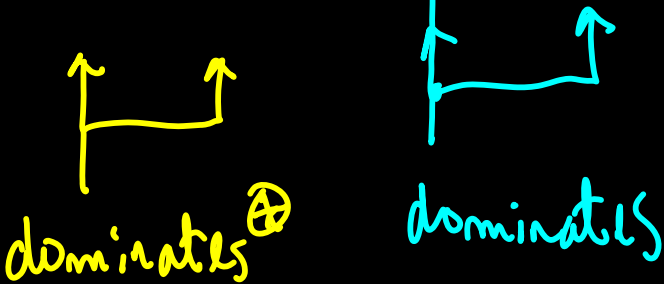

(\*) the  $m_{12}$  column tells us that we need  $0X100$ .

Since this PI also covers  $m_4$ , we don't need the  $m_4$  column.

### Summary

1. Generate all PIs from minterms through iterative combining
2. Create a cover table, and identify Ess. PIs.
3. if there are uncovered minterms, make a reduced cover table.
4. Use row/column dominance to reduce the cover table.

5. Identify new "Ess.  $PI_s$ ".

6. Iterate from step 3.

Note: It may be necessary to make "arbitrary" choices at the end. Example:

	$m_i$	$m_j$	$m_k$
$PI_A$	✓	✓	
$PI_B$		✓	✓
$PI_C$	✓		✓

- look at all combinations (branch & bound)

Using  $\ast$ -operation and  $\#$ -operation for minimization

$\ast$ -operation

- consider two 0-cubes (minterms)  $A = 010, B = 110$

$A = 010 \quad A_1 \quad A_2 \quad A_3$

$B = 110 \quad B_1 \quad B_2 \quad B_3$

- two step  $\ast$ -operation process:

(1) Use Table

$A_i \backslash B_i$	0	1	X
0	0	0	0
1	0	1	1
X	0	1	X

intuition: the  $\ast$ -op table returns what  $A_i, B_i$  have "in common"

For our example  $A_1 * B_1 = 0 * 1 = \emptyset$

$$A = 010$$

$$B = 110$$

$$A_2 * B_2 = 1 * 1 = 1$$

$$A_3 * B_3 = 0 * 0 = 0$$

Step 2: form the overall result  $C = A * B$

Two cases: 1.  $C = \emptyset$  if  $A_i * B_i = \emptyset$  for more than one  $i$ .

2. Otherwise

$$C_i = A_i * B_i \text{ when } \neq \emptyset$$

$$C_i = x \text{ when } = \emptyset$$

Example:

$$A = 1x0, B = 1x1$$

$$A_1 * B_1 = 1$$

$$A_2 * B_2 = x$$

$$A_3 * B_3 = \emptyset$$

Case 2:  $C = 1xx$

Algebraically:  $A = x_1 \bar{x}_3$

$$B = x_1 x_3$$

$$A + B = x_1$$

Example:

$$A = 0x0$$

$$B = 1x1$$

$x_1 x_2$		$x_3$			
$x_3$		00	01	11	10
	0	1	1		
1				1	1

$$C = A * B = \emptyset$$

Example:  $A = 0x0$

$B = x11$

$$\therefore C = A * B$$

$$= 01x$$

$$A_1 * B_1 = 0$$

$$A_2 * B_2 = 1$$

$$A_3 * B_3 = \phi$$

$x_1, x_2$		00	01	11	10
$x_3$	0	1	1		
	1		1	1	

- The  $*$ -operation can be used to generate all implicants, and therefore all prime implicants.

$$f(x_1, \dots, x_4) = \{ \underline{x x 0 0}, \underline{1 1 0 x}, \underline{1 x 1 1}, \underline{1 0 x 0} \}$$

$G_i$		0	1	x
$A_i$	0	0	$\phi$	0
	1	$\phi$	1	1
	x	0	1	x

$x_1, x_2$		00	01	11	10
$x_3, x_4$	00	1	1	1	1
	01			1	
	11			1	1
	10				1

$$110x * 1x11 = 11\phi 1$$

$$11x1$$

$$1x11 * 10x0 = 10|\phi$$

$$101x$$

Procedure for using  $*$ -op to find All PIs

- let  $C^k$  be a cover (set of cubes) for a function
- generate a new set of cubes  $G^{k+1}$  by finding  $*$ -op for all pairs of cubes  $c^i, c^j$ .


$$G^{k+1} = C^i * C^j \quad \forall C^i, C^j \quad i \neq j$$

- then  $C^{k+1} = C^k \cup G^{k+1}$  - (redundant cubes)

- repeat until  $C^{k+1} = C^k$

Example  $f = m(1, 3, 5, 6, 7)$

$$C^0 = \{001, 011, 101, 110, 111\}$$

 

$$\therefore G' = \{0x1, x01, x11, 1x1, 11x\}$$

$$C' = C^0 \cup G' - (\text{redundant})$$

$$C' = G'$$

- Repeat:  $C' = \{0x1, x01, x11, 1x1, 11x\}$



$$G^2 = \{001, 011, x x 1, x 1 1, 101, 1 x 1, 111\}$$

$$C^2 = C^1 \cup G^2 - (\text{redundant})$$

$$C^2 = \{ \underline{x x 1}, \underline{1 1 x} \}$$

~repeat

$$G^3 = 111$$

$$C^3 = C^2 \cup G^3 - (\text{redundant}) = C^2 \quad \text{Done!}$$

check:

$x_1 x_2$		00	01	11	10
$x_3$	0			1	
	1	1	1	1	1

$11x$  (vertical oval)  
 $xx1$  (horizontal oval)

$$f = m(1, 3, 5, 6, 7)$$

Problem: design a cdt for which  $f=1$  iff

- $(x_1 = x_2)$  and  $(x_3 = x_4)$ , but  $x_1 \neq x_3$  or
- $(x_1 = x_3)$  and  $(x_2 = x_4)$ , but  $x_1 \neq x_2$  or
- $x_1 = x_4 = 1$
- $x_1 = 1, x_2 = x_3 = x_4 = 0$

$$C^0 = \{0011, 1100, 0101, 1010, 1xx1, 1000\}$$



$$C^0 = \begin{pmatrix} 0011 \\ 1100 \\ 0101 \\ 1010 \\ 1xx1 \\ 1000 \end{pmatrix}$$

$$G^1 = \begin{pmatrix} x011 \\ 110x \\ 1x00 \\ x101 \\ 101x \\ 10x0 \\ 100x \end{pmatrix}$$

$$C^1 = \begin{pmatrix} 1xx1 \\ x011 \\ 110x \\ 1x00 \\ x101 \\ 101x \\ 10x0 \\ 100x \end{pmatrix}$$

(skip redundant)


$$G^2 = \begin{pmatrix} 1x0x \\ 10xx \end{pmatrix}$$

$$C^2 = \begin{pmatrix} 1xx1 \\ 1x0x \\ 10xx \\ x011 \\ x101 \end{pmatrix}$$

Then, we would find that

$$C^3 = C^2 \quad \text{Done}$$

PTs

 

$$C^0 = \{0011, 1100, 0101, 1010, 1xx1, 1000\}$$

- In this process we need a way of identifying redundant cubes

## #-Operation

- While  $\#$ -op identifies the common parts of cubes, the  $\#$ -op identifies how cubes "differ".

$\#$ -op  $A \# B$  yields the part of  $A$  that is not covered by  $B$ .

Example:

$$A = 11x, B = xx0$$

$$11x \# xx0 = 111$$

$x_1 x_2$	00	01	11	10
$x_3$	0	1	1	1
1	0	0	1	0

$$xx0 \# 11x = 0x0, x00$$

Step 1: Find coordinate  $\#$ -op  $C_i = A_i \# B_i$  using

table:

$A_i \backslash B_i$	0	1	x
0	$\emptyset$	$\emptyset$	$\emptyset$
1	$\emptyset$	$\emptyset$	$\emptyset$
x	1	0	$\emptyset$

Case 1:  $A$  is not covered at all by  $B$

	00	01	11	10
0	1	1		
1			1	1

$$A = 0x0 \quad A \# B = \emptyset \emptyset \emptyset$$

$$B = 1x1 \quad B \# A = \emptyset \emptyset \emptyset$$

Rule 1: if  $A_i \# B_i = \emptyset$  for any  $i$ , then  $C = A \# B = A$

Case 2: A is fully covered by B

	00	01	11	10
0		1	1	
1		1	1	

$$A = 11x$$

$$B = x1x$$

$$A \# B = \varepsilon \varepsilon \varepsilon$$

Rule 2: When  $A_i \# B_i = \varepsilon \forall i$ , then  $C = A \# B = \phi$

Case 3: part of A is covered by B

	00	01	11	10
0		1	1	
1		1	1	

$$A = x1x$$

$$B = 11x$$

$$01x$$

- from the table,  $A \# B = 0 \varepsilon \varepsilon$

Example (Case 3):  $A = 11x$ ,  $B = xx0$  Table:  $\varepsilon \varepsilon 1$

$$C = 111$$


$$A = xx0, B = 11x$$

$000 \rightarrow 0x0 \checkmark$   
 $010$   
 $100 \rightarrow x00 \checkmark$   
 $110$

Rule 3: When calculating  $C = A \# B$ , for each  $i$  in which  $A_i = x$  but  $B_i \neq x$ , there will be a cube produced. In this cube  $C_i = B_i$  and all other digits from A.

 Example:  $A = \begin{matrix} \downarrow & \downarrow & \downarrow \\ \underline{xxx} & 1 \end{matrix}$   
 $B = \underline{\underline{110x}}$

$C = A \# B$   
 $= \left\{ \begin{matrix} 0xx1 \\ x0x1 \\ xy11 \end{matrix} \right\}$



# Using #-op to Identity Redundant Cubes

- given  $C^K = \{0x0, 00x, 100, 0xx\}$
- to check if a cube  $\rho^i$  is redundant

$$\rho^i \# \rho^j = \emptyset, \text{ for any } i \neq j$$

- in this example:

$A_i \backslash B_i$	0	1	x
0	2	2	2
1	2	2	2
x	1	0	2

$\rho^i = 0x0$

$0x0 \# 00x = 212 \neq \emptyset$
$0x0 \# 100 = \emptyset \neq \emptyset$
$0x0 \# 0xx = 222 = \emptyset \text{ Red!}$

$\rho^i = 00x$

$00x \# 0x0 = 221 \neq \emptyset$
$00x \# 100 = \emptyset \neq \emptyset$
$00x \# 0xx = 222 = \emptyset \text{ Red!}$

etc. ! (100, 0xx are NOT Red.)

## Complete Procedure for Find a minimal Cover

1. Use  $\nabla$ -op to find all implicants, and remove redundant cubes using  $\#$ -op  $\Rightarrow$   $PIs$ .
2. Using  $\{PIs\}$ , identify which ones are Essential.

Recall: an Ess.  $PI$  covers at least one minterm not covered by any other  $PI$ .

~ Given a cover consisting of  $PIs$

$C^k = \{PIs\}$ , and  $p^i$  is a cube in that set, to check if  $p^i$  is essential

$$p^i \# (C^k - p^i) \neq \emptyset$$

e.g.  $C^k = \{p^1, p^2, p^3, p^4\}$

To check if  $p^2$  is essential:

$$\left( (p^2 \# p^1) \# p^3 \right) \# p^4 \neq \emptyset$$

Example:  $C^k = \{ \underline{0x0}, 01x, x11, 1x1 \}$


1.  $0x0 \# 01x = 000 \# x11 = 000 \# 1x1 = 000 \therefore$  essential!

2.  $01x \# 0x0 = 011 \# 1x1 = \emptyset \therefore$  not essential.

... etc.


3. Include the Ess. PTs in the cover. If all minterms of the function are covered, then done.
4. Choose additional PTs to cover the minterms.

## Branch & Bound

 

## Incorporating Don't Cares

 Example:  $f$  has ON-set =  $\{000x, x111\}$   
 DC-set =  $\{1x0x\}$



Step 1: Use  $C^0 = \{ON\text{-set}\} \cup \{OC\text{-set}\}$  to find  $PIs$ ,  
using  $*$ -op (and  $\#$ -op for removing redundant cubes).

Note: resulting PIs should be checked (with #op) to make sure that they cover at least one ON-set minterm, and not just DC-set minterms.

Here,  $PI_1 = \{X00X, X111, 11X1, \cancel{1X0X}^{DC!}\}$

Step 2: find Ess. PIs.

$$\left( \left( \left( \rho^2 \# \rho' \right) \# \rho^3 \right) \# \rho^4 \right) \# \{DC\text{-set}\}$$

Example:  $||x| \# x00x = ||x| \# x|| = ||0| \# |x0x = \emptyset$   
 $\therefore$  not CSS.

## Ranking of Assign #1:

Input format is flexible? 0-1

Intermediate results displayed? 0-1

output format is readable? 0-2?

All minimal sol's found? 0-2

Thoroughness of testing: 0-2

Code Structure: 0-2

Code uses sensible variable names & comments: 0-2

Run time: 0-1

## Multilevel Representation of Logic Functions

Example: Implement a function  $f$  that is 1 when (at least one of inputs  $x_1, x_2$  is equal to 1) and (both  $x_3, x_4$  are 1). Also,  $f$  is 1 if ( $x_1 = x_2 = 0$ ) and either ( $x_3, x_4$  is 1).

$$f = (x_1 + x_2)(x_3 x_4) + \bar{x}_1 \bar{x}_2 (x_3 + x_4)$$

Note:  $\underline{\bar{a}bc} + \underline{\bar{a}}(\underline{b} + \underline{c})$

ab		00	01	11	10
c	0			1	
	1		1	1	1

$$= bc + a(bc)$$

$$f = (x_3 x_4) + \bar{x}_1 \bar{x}_2 (x_3 + x_4)$$

- Assume we have a second function  $f_2$  which is equal to 1 in all cases except when (both  $x_1, x_2$  are 0) or (both  $x_3, x_4$  are 0)


$$\bar{f}_2 = \bar{x}_1 \bar{x}_2 + \bar{x}_3 \bar{x}_4$$

$$\therefore f_2 = (x_1 + x_2)(x_3 + x_4)$$



$$f = (\chi_3 \chi_4) + \overline{\chi_1} \overline{\chi_2} (\chi_3 + \chi_4)$$
 
$$= (\chi_3 \chi_4) + (\overline{\chi_1} + \overline{\chi_2}) (\chi_3 + \chi_4)$$



Example:  $f = \sum m(4, 7, 9, 10, 12, 13, 14, 15)$

$\chi_3 \chi_4 \backslash \chi_1 \chi_2$	00	01	11	10
00		1	1	
01			1	1
11		1	1	
10			1	1

$$f = \chi_2 \overline{\chi_3} \overline{\chi_4} + \chi_1 \overline{\chi_3} \chi_4 + \chi_2 \chi_3 \chi_4 + \chi_1 \chi_3 \overline{\chi_4}$$

$$\text{Cost} = \# \text{ gates} + \# \text{ gate-inputs}$$

$$= 5 + 16 = 21$$

## Functional Decomposition

- Find subfunctions of some, but not all, of the variables that we can use in a multilevel expression.
- Example: find subfunction of  $\chi_3, \chi_4$

$$f = x_2 \bar{x}_3 \bar{x}_4 + x_1 \bar{x}_3 x_4 + x_2 x_3 x_4 + x_1 x_3 \bar{x}_4$$


$$= x_1 (\bar{x}_3 x_4 + x_3 \bar{x}_4) + x_2 (\bar{x}_3 \bar{x}_4 + x_3 x_4)$$

Now, subfunction  $g = \bar{x}_3 x_4 + x_3 \bar{x}_4 = x_3 \oplus x_4$

then  $\bar{g} = \bar{x}_3 \bar{x}_4 + x_3 x_4 = x_3 \odot x_4$

→  $f = x_1 g + x_2 \bar{g}$

$g = x_2 \bar{g} + x_1 g$  ← same

 

Cost: 5 gates + 9 = 14 < 21

Deriving the multilevel expression from k-map

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00		1	1	
01			1	1
11		1	1	
10			1	1

$x_3 x_4 \mid g$	
00	0
01	1
10	1
11	0

$g = x_3 \oplus x_4$ . The function  $f$  is defined by  $g$  when  $x_1 x_2 = 10$ . So, this is  $g \cdot x_1 \bar{x}_2$ . The second column is  $\bar{g}$ , and represents this part of  $f$ :  $\bar{g} \cdot \bar{x}_1 x_2$ . The column 11 is

$$(1) \cdot x_1 x_2 \therefore f = g x_1 \bar{x}_2 + \bar{g} \bar{x}_1 x_2 + x_1 x_2$$

- We can think of this as a 2-level expression of a 3-variable function  $h[x_1, x_2, g]$

$$\therefore f(x_1, x_2, x_3, x_4) = h[x_1, x_2, g(x_3, x_4)]$$

- We can optimize  $h$

$$g = x_2 \bar{x}_3 + x_1 x_3 \therefore g = x_2 \bar{g} + x_1 g$$

Example

$x_3, x_4$		$x_1, x_2$			
		00	01	11	10
		00	1		
	01			1	1
	11	1			
	10		1	1	1

$$x_5 = 0$$

$x_3, x_4$		$x_1, x_2$			
		00	01	11	10
		00			
	01	1	1	1	1
	11				
	10	1	1	1	1

$$x_5 = 1$$

$$g = x_1 + x_2 + x_5$$

Example: explore subfunctions of  $x_1, x_2, x_5$

- The part of  $f$  represented by  $g$  is

$$g \cdot (\bar{x}_3 x_4 + x_3 \bar{x}_4) = g \cdot (x_3 \oplus x_4)$$


- The part of  $f$  represented by  $\bar{g}$  is

$$\bar{g} \cdot (x_3 \odot x_4)$$

$$\therefore f = g(x_3 \oplus x_4) + \overline{g(x_3 \oplus x_4)}$$

$$\text{— let } k = x_3 \oplus x_4$$
 
$$\begin{aligned} \text{Then, } f &= gk + \overline{g}\overline{k} \\ &= \overline{(g \oplus k)} = g \odot k \end{aligned}$$




## Binary Decision Diagrams (BDDs)

Def'n: a BDD is a graph that represents a logic function. For a specific order of variables, a BDD is a canonical representation.


Example:

$x_1, x_2$	$f$
00	1
01	0
10	1
11	1


## Decision Tree

 

 ① merge identical nodes, starting from the bottom



②. Remove redundant nodes

 


BDD <sup>⊗</sup>


⊗ BDD, a.k.a. Reduced Ordered BDD

AND, OR, XOR BDDs

$f = x_1 x_2$


 


$f = x_1 + x_2$

 

$f = x_1 \oplus x_2$

① Merge

  

$$f = x_1 \oplus x_2 \oplus x_3$$

